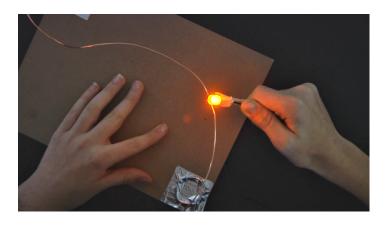




MAKE IT!: STEADY HAND GAME



Subjects:

- Circuitry
- Engineering
- Crafting

INTRODUCTION

It takes nerves of steel to get down the copper! Will your wand touch the copper path and light up the LED? Also a fun eyehand coordination game, this project is an exploration into conductivity, introduction to electric circuits, and intro to LEDs.

WHAT WE'LL BE USING:

- 10mm LED
- CR2032 3V Coin Battery
 craft stick
- Aluminum tape
- 14 Gauge bare copper wire Masking Tape
- 18 Gauge insulated stranded wire
- 81/2" x 11" Chipboard
- Scissors
- Ruler
- Needle Nose Pliers

WHY DOES IT WORK?

A circuit is a path that electricity (or electrons) flow through. We are connecting an electricity source, the battery, to different conductive components, things that let the electrons pass through them.

The circuit is not complete until the wire on the wand touches the copper wire, and the LED bulb lights up.

Standards:

- PS3.D
- ETS1.A
- ETS1.C

nextgenscience.org

Maker **Capacities:**

- Tinker to **Explore**
- Finding Opportunities

agencybydesign.org

Key Terms

- Circuit
- LED
- Conductive
- Switch







